

Background and Goals

Today we will apply our knowledge of 2nd order linear ODE to some questions about electrical circuits. An “RLC circuit” is one that contains a voltage source $v_T(t)$ (time dependent), a *resistor* (i.e. something that *dissipates electrical energy*) with resistance R , an *inductor* (a device or component that *stores magnetic energy*) with inductance L , and a *capacitor* (a device or component that *stores electrical energy*) with capacitance C . Many basic electrical circuits have this form.

It can be shown that the voltage change across the capacitor, written v_C , satisfies the 2nd order ODE

$$(1) \quad LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = v_T(t)$$

so that these circuits are also described by the harmonic oscillator equations that we have been studying for the past week. We will always consider a *periodic, sinusoidal* voltage source (“forcing”) term

$$v_T(t) = a \sin(\omega t).$$

Maple Notes

All of the plots necessary for this lab will be generated using the basic Maple `plot` command. However, if you want to check your results, you can also use the `DEplot` command from Lab 1 to plot approximate numerical solutions to 2nd order ODE as follows. For example, say we want to see the solution of the initial value problem

$$\begin{cases} 4 \frac{d^2 y}{dt^2} + 3 \frac{dy}{dt} + 10y = 3 \cos(2t) \\ y(0) = 5 \\ y'(0) = -3 \end{cases}$$

Then the following commands could be used. First load the `DEtools` package with:

```
with(DEtools):
```

Then define the ODE with:

```
eqn:=4*diff(y(t),t$2)+3*diff(y(t),t)+10*y(t) = 3*cos(2*t);
```

and plot the solution for $t \in [0, 10]$ with

```
DEplot(eqn,y(t),t=0..10,[[y(0)=5,D(y)(0)=-3]]);
```

As in Lab 1, adjusting the `linecolor` and `stepsize` options, the range of t -values, etc. will often be necessary to get reasonable, printable graphs.

Lab Questions

- A) (A worked example) Suppose we want to understand the voltage in an RLC circuit with $R = 1000$, $L = 2$, and $C = 10^{-6}$, and a voltage source $v_T = 20 \sin(500t)$. We know that the general solution of (1) in this case:

$$(2) \quad (2 \times 10^{-6}) \frac{d^2 v_C}{dt^2} + (10^{-3}) \frac{dv_C}{dt} + v_C = 20 \sin(50t)$$

looks like $v_C(t) = c_1 v_1(t) + c_2 v_2(t) + v_p(t)$, where $c_1 v_1(t) + c_2 v_2(t)$ is the general solution for the homogeneous equation

$$(2 \times 10^{-6}) \frac{d^2 v_C}{dt^2} + (10^{-3}) \frac{dv_C}{dt} + v_C = 0$$

and $v_p(t)$ is any particular solution.

- 1) To find $v_1(t), v_2(t)$, we find the roots of the characteristic polynomial of the corresponding first order system:

$$(2 \times 10^{-6}) \lambda^2 + (10^{-3}) \lambda + 1 = 0$$

To find them using Maple, enter:

```
fsolve(2*10^(-6)*lambda^2+10^(-3)*lambda+1,lambda,complex);
```

- 2) Call the roots $\alpha \pm i\beta$. Then we know that the general solution of the homogeneous equation has the form $c_1 e^{\alpha t} \cos(\beta t) + c_2 e^{\alpha t} \sin(\beta t)$. Define the two terms here as functions in Maple using:

```
v1:= t->exp(alpha*t)*cos(beta*t);  
v2:= t->exp(alpha*t)*sin(beta*t);
```

(You will need to assign values to `alpha` and `beta` or fill in the correct numerical values.)

- 3) Now, we need to find a particular solution v_p . This is where the method of undetermined coefficients that we discussed in class earlier comes in. The $20 \sin(50t)$ term on the right means that we guess that a particular solution will have the form $v_p(t) = A \cos(50t) + B \sin(50t)$. (Note, no term here is a solution of the homogeneous equation, so we *do not need a t^s factor, that is, $s = 0$.*) Plug $v_p(t)$ into (2) and determine the values of A, B to yield a solution. You should get:

$$\begin{aligned} .995A + .05B &= 0 \\ -.05A + .995B &= 20 \end{aligned}$$

So $A \doteq -1.007$ and $B \doteq 20.05$. You can find these equations and the solutions in Maple using

```

vp:=t->A*cos(50*t)+B*sin(50*t);
2.0*10^(-6)*diff(vp(t),t$2)+1.0*10^(-3)*diff(vp(t),t)+vp(t);
ABSol := fsolve({.995*A+.05*B,-.05*A+.995*B-20},{A,B});
vpp := t -> subs(ABSol,vp(t));

```

The last line defines the particular solution as a new function, with the values of A, B “plugged in.”

- 4) Now, we find the values of c_1, c_2 that give a solution of the initial value problem with $v(0) = 0, v'(0) = 1$. Here are some sample Maple commands to work with:

```

vC:=t->c1*v1(t)+c2*v2(t)+vpp(t);
initeqs:={vC(0)=0,subs(t=0,diff(vC(t),t))=1};
cvals:=fsolve(initeqs,{c1,c2});

```

- 5) Finally, plot the solution of (2) with $v_C(0) = 0$, and $v'_C(0) = 1$. (Note: You’ll need to think about an appropriate interval of t values for your plot. A term like $\cos(661.437t)$ is oscillating really fast!) Also plot the “transient” part of the solution separately. (This should show you why the solution of (2) looks virtually indistinguishable from a sinusoidal function!)

- B) Suppose $L, C > 0$, but the resistance $R = 0$. (This is a very, very idealized situation, of course, even better than “superconductivity.”) What do the solutions of (1) look like in this case? Derive analytic formulas by our *undetermined coefficients* technique for inhomogeneous 2nd order equations. Be sure to distinguish between the two different cases:

- 1) $i\omega$ is not a root of the characteristic polynomial, and
- 2) $i\omega$ is a root of the characteristic polynomial.

How is the analytic form of the solution different in these two cases?

- C) Using Maple, plot the analytic solutions of (1) with $R = 0, C = 10^{-6}, L = 1, a = 1, v_C(0) = 1, v'_C(0) = 0$, and $\omega = 900, 950, 1000, 1050, 1100$ (five graphs in all). (You’ll need to choose your t interval carefully to get informative graphs!) The name for the $\omega = 1000$ case is *resonance*. Describe what a resonant solution does as $t \rightarrow \infty$. Can you think of a “real world” situation that might correspond to resonance? Is it a “good” or a “bad” thing to have a resonant solution?

- D) Next, we will study the more realistic case $R > 0$. By considering the form of the roots of the characteristic polynomial of the 1st order system, show that if $R > 0$, then every solution of the corresponding homogeneous equation

$$LC \frac{d^2 v_C}{dt^2} + RC \frac{dv_C}{dt} + v_C = 0$$

tends to *zero* as $t \rightarrow \infty$. These terms in the general solution of (1) are called “transients” for this reason.

- E) Plot and describe the solutions for fixed $a = 10$ and $\omega = 1000, 1200, 1400, 1600, 1800, 2000$ with $R = 2000$, $C = 2 \times 10^{-7}$, and $L = 1.5$. How does the amplitude of the steady state solution compare with the amplitude of the forcing term (as a function of ω)? Does resonance occur in this situation? Explain.

Assignment

Individual write-ups giving answers to the above questions. **Due:** In class, Friday, November 5.